Tai Duc Nguyen - ECEC471 - 10/20/2019

Lab Report Week 3

CMOS NOR & NAND

Content

- · Objective
- Introduction
 - Gate sizing
 - · Rise time and Fall time
 - Propagation delay
 - Symmetric gates
- · Simulation process and results
 - Schematic design
 - · Layout design of symmetric inverter
 - Physical verification
- Analysis of simulation results
- Conclusion

Objective

The objective for this laboratory is to design, simulate and verify the schematic and layout of a 2 input CMOS NOR & a 2 input CMOS NAND gate using Cadence Virtuoso. The process includes: 1. Creating the schematic with known sized PMOS & NMOS 2. Obtain a symmetric version of each gate with the ADE(L) simulation coupled with parametric analysis. 3. With the sizing decided for the NMOS & PMOS, the layout of each gate is built and checked against DRC and VLS verification tool.

Introduction

NOR gate and NAND gate are Universal gates, which means that they are the building block of many, if not most, advanced electronics. Both gates require a pull up network consisting of 2 PMOS and a pull down network consisting of 2 NMOS. In a NOR gate, the 2 PMOS are connected in series and the 2 NMOS are connected in parallel. In a NAND gate, however, the reverse happens, where the PMOSes are in parallel and the NMOSes are in series.

Gate sizing

The sizing of the PMOS and NMOS components in each gate have great impact to the performance of the gates. Hence, it is important to make both gate symmetric (equal rise time and fall time) to create a reponsive device.

Rise time and Fall time

The Rise time (denoted as t_r) is the time required for the output signal voltage to rise from 10% to 90%.

The Fall time (noted as t_f) is the time required for the output signal voltage to fall from 90% to 10%.

Propagation delay

Propagation delay (denoted as t_{pd}) is the time from the moment the input voltage reaches 50% to the time the output voltage also reaches 50%.

Symmetric gates

A gate is considered symmetric if and only if $t_r=t_f$. Hence, both the low to high and high to low transition will meet at $\frac{1}{2}$ VDD. In order to obtain this symmetricity, the sizing of the width of the NMOS and PMOS components can be adjusted.

Simulation process and results

Schematic design

The following figure (1a & 1b) show the initial set up for the schematic of the NOR gate (1a) and NAND gate (1b). All the lengths are 50nm and widths are 90nm.

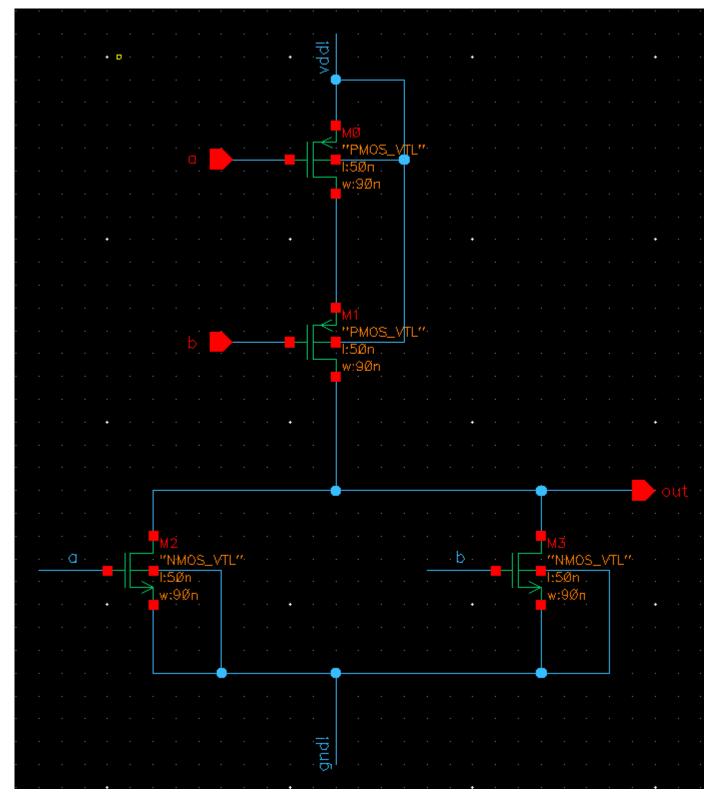


Figure 1a: NOR gate initial schematic

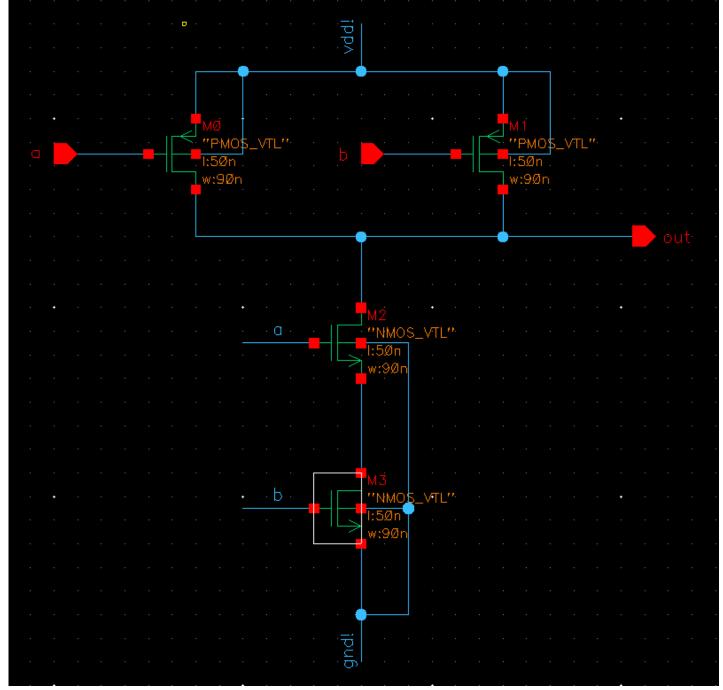


Figure 1b: NAND gate initial schematic

To simulate the transient and DC behavior of each gate, a 5fF capacitive load and a voltage source (Amplitude=1.2V, delay=0, rise time=5ps, fall time=5ps, time period (input a)=2ns, time period (input b)=4ns, pulse width (input a)=1ns, pulse_width (input b)=2ns). The top level schematic for NOR gate (Figure 2a) and NAND gate (Figure 2b) is shown below:

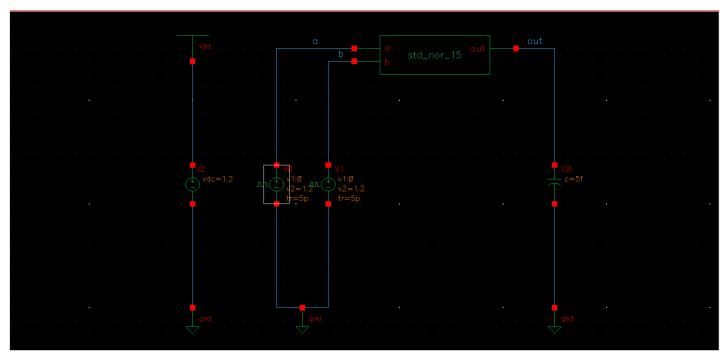


Figure 2a: NOR gate initial top level schematic

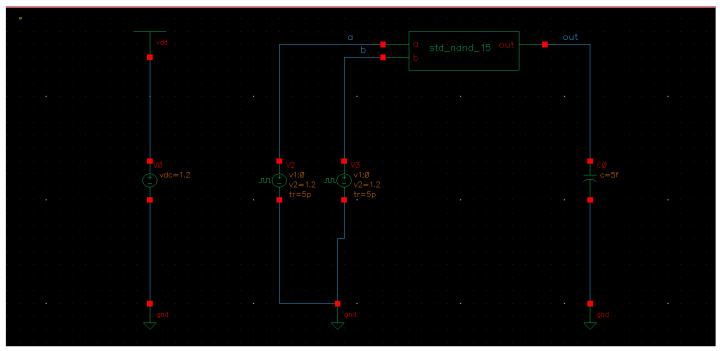


Figure 2b: NAND gate initial top level schematic

Hence, the transient behavior of each gate (Figure 3a, 3b) and the DC behaviors (Figure 4a, 4b) can be recorded and shown:

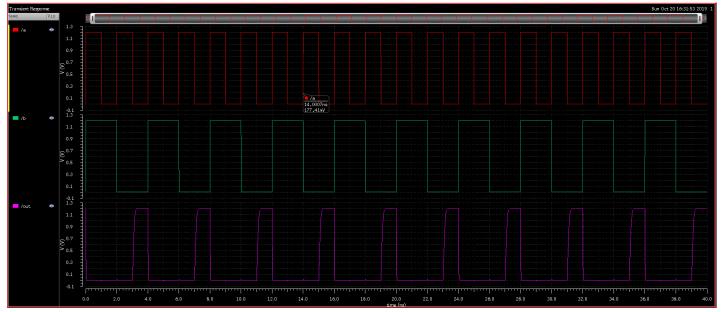


Figure 3a: NOR gate initial transient plot

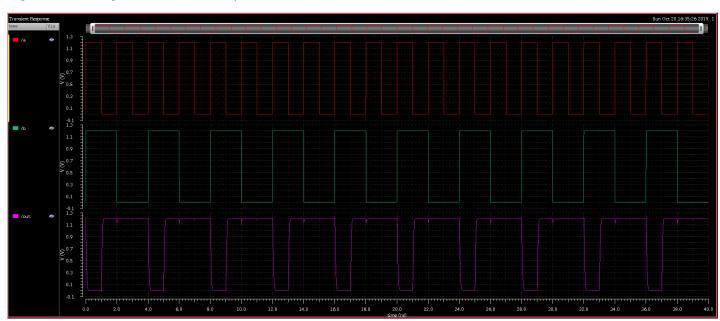


Figure 3b: NAND gate initial transient plot

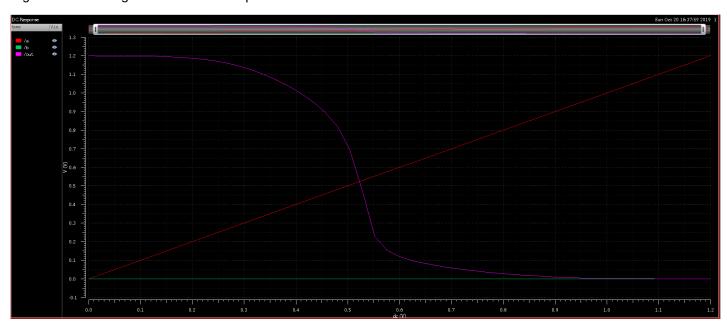


Figure 4a: NOR gate initial DC plot

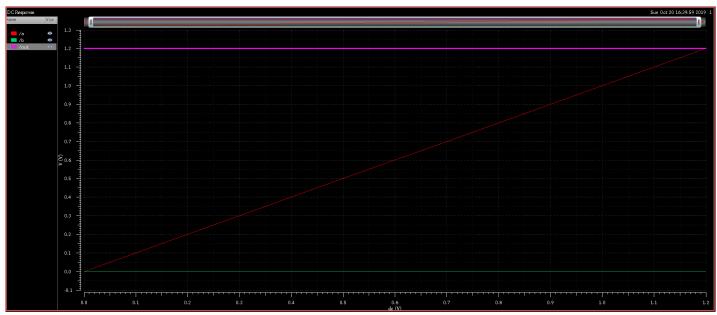


Figure 4b: NAND gate initial DC plot

From these simulations, it is apparent that both the initial sizing does not lead to a symmetric device – the switching potential is not at $\frac{1}{2}$ VDD (0.6V). The DC plot for the NOR gate shows that the switching potential is < 0.6V, which means that the width of the PMOS needs to be increase. However, the DC plot for the NAND gate indicates that there is no switching potential, which means that the width of the NMOS is too small.

To do the parametric analyses for both gates, it is important to consider the worse-case scenario with regards to the propagation delay. For the NOR gate, there are 2 combination of input signals that will induce a change in the output signal – when b=0 and a transition from 1->0; and when both a & b transition from 0->1. Measuring the propagation delay and choose the combination with the longest t_{pd} (Figure 5a). This combination will allow the alteration of the top level schematic and the work on the parametric analysis.

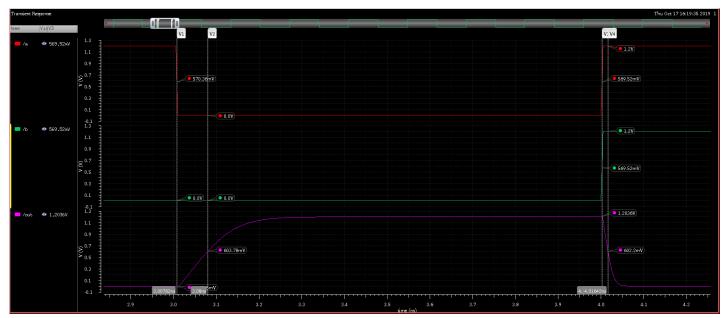


Figure 5a: NOR gate worse-case propagation delay analysis

From Figure 5a, it is clear that the combination of when b=0 and a transition from 1->0 will produce the longest t_{pd} .

$$t_{a=1->0,b=0}=3.08000-3.00762=0.07238ns$$

$$t_{a=0->1,b=0->1} = 4.01642 - 4.00300 = 0.01342ns$$

Therefore, the modified top level schematic is:

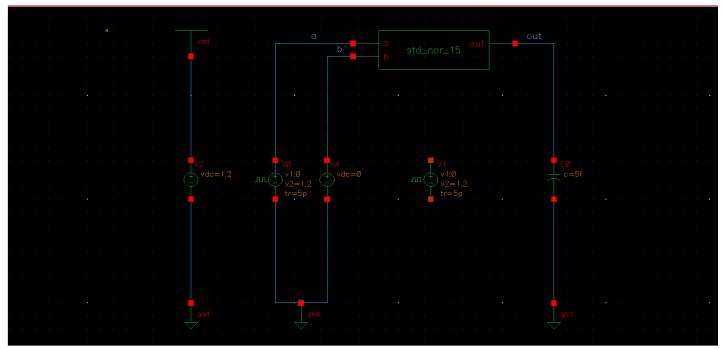


Figure 5b: NOR gate modified top level schematic

Similarly, the NAND gate's worse-case scenario t_{pd} analysis is conducted and it's concluded that the combination of both inputs going from 0->1 will produce the longest propagation delay (Figure 5c).

$$t_{a=1->0,b=1} = 9.049224 - 9.007371 = 0.041853ns$$

$$t_{a=0->1,b=0->1} = 12.05000 - 12.00248 = 0.04752ns$$

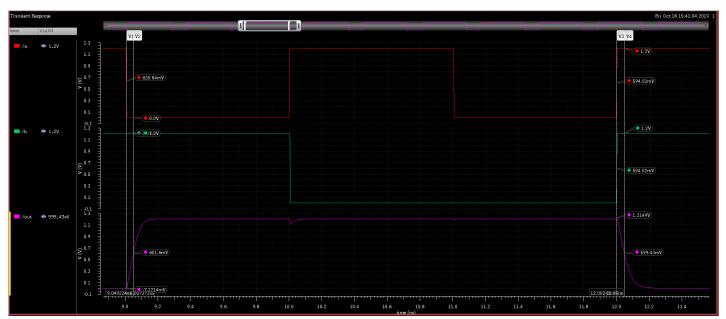


Figure 5c: NAND gate worse-case propagation delay analysis

Therefore, the modified top level schematic is:

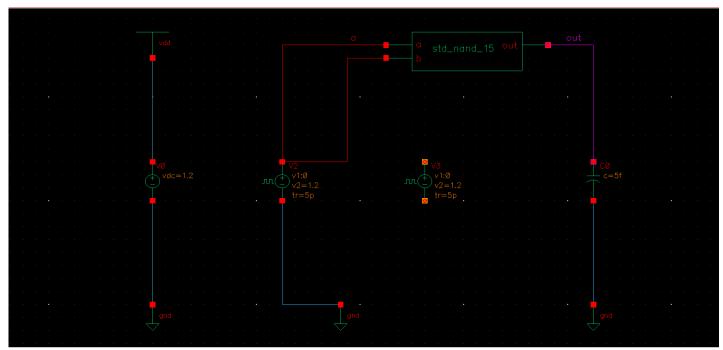


Figure 5d: NAND ggate modified top level schematic

With regards to the NOR gate, a parametric analysis is conducted (Figure 6a), performing the DC plot on different values of the PMOS's widths, from 90nm to 300nm. The result is that: when the PMOS's width is at approximately 156nm, then the switching potential is 0.6V. Due to software constraint (Rule Grid.1-6), the chosen PMOS width is 155nm.

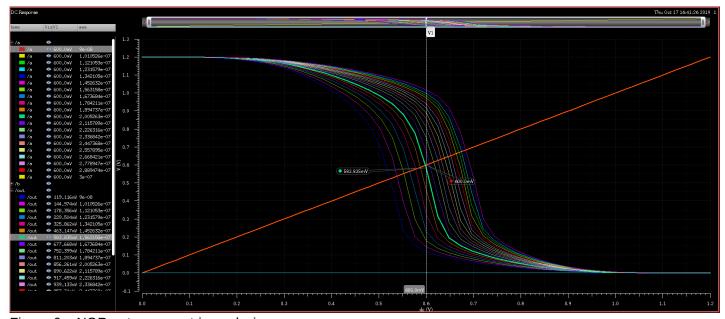


Figure 6a: NOR gate parametric analysis

The parametric analysis for the NAND gate cannot be conducted if the NMOS width is not increased since there won't be any PMOS width (> 90nm) that produce the switching potential of 0.6V. Therefore, when the NMOS width is chosen to be 200nm, the PMOS width of 90nm results in a symmetric device (Figure 6b).

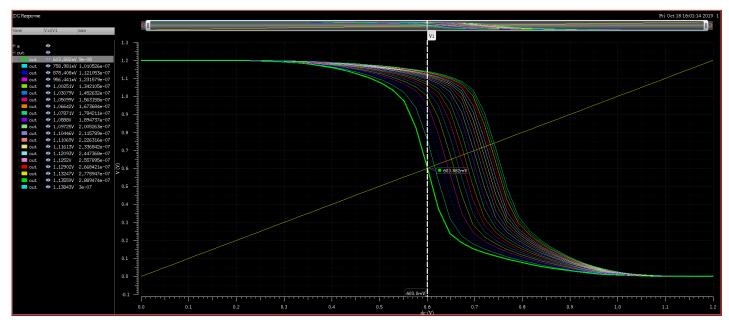


Figure 6a: NAND gate parametric analysis

After the parametric analysis is conducted and resulting widths for the NMOS and PMOS components of each gate are decided, the final schematics of the NOR and NAND gate are (Figure 7a, 7b):

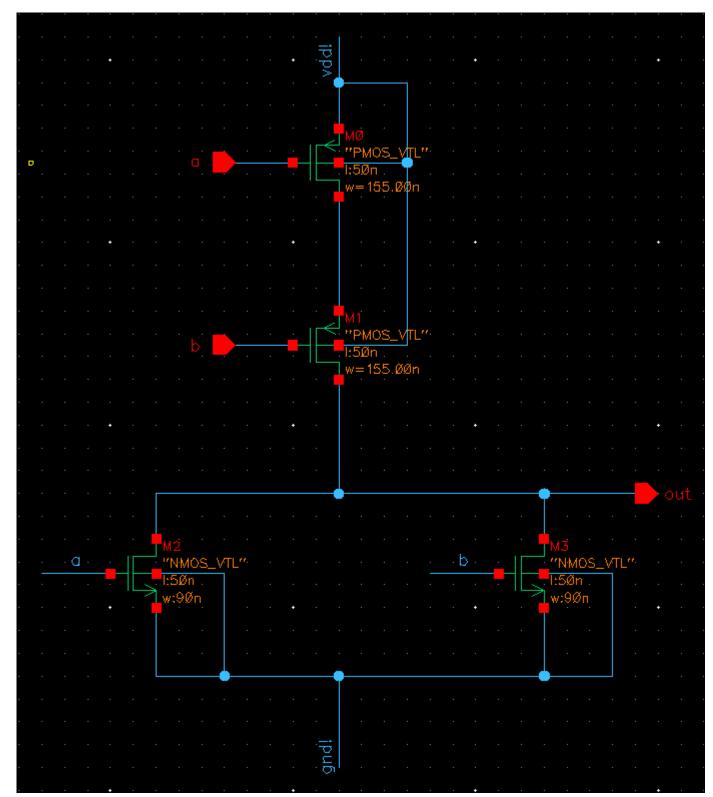


Figure 7a: NOR gate final schematic

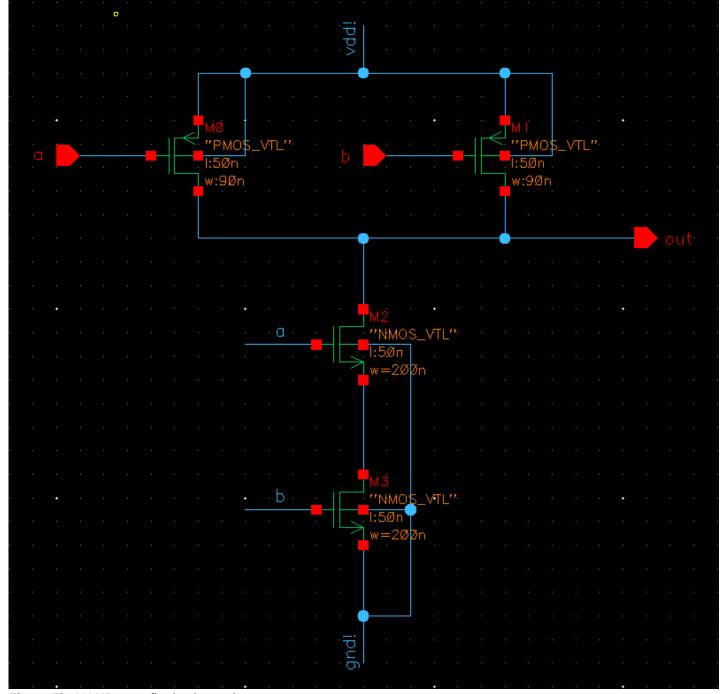


Figure 7b: NAND gate final schematic

Finally, the design can be concluded with an analysis of the rise/fall time of both devices (Figure 8a, 8b):

$$t_{rNOR} = 13.09148 - 13.01852 = 0.07296$$

 $t_{fNOR} = 14.07627 - 14.00903 = 0.06724$
 $t_{rNAND} = 7.05552 - 7.01354 = 0.04198$
 $t_{fNAND} = 8.05000 - 8.00848 = 0.04152$

It is apparent that $t_{rNOR} \neq t_{fNOR}$, this is because of the design constraint of the software. It is not possible to have a width of 156.31nm; 155nm is chosen instead.

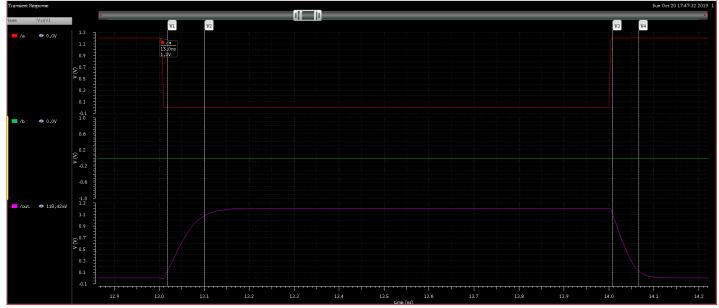


Figure 8a: NOR gate final rise and fall time

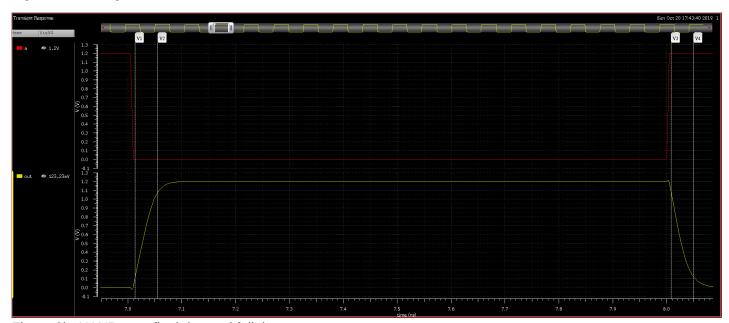


Figure 8b: NAND gate final rise and fall time


Layout designs of symmetric NOR and NAND gates

The schematic of the symmetric NOR and NAND gates is finalized in the previous section. The physical layouts of the gates are created with the software: Virtuoso Layout Suite L.

Using stick diagrams for the 2 gates:

LAYOUTS

The CMOS NOR Gate

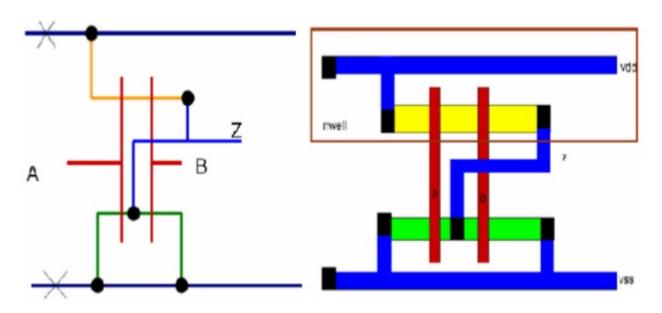


UNIT - II CIRCUIT DESIGN PROCESSES

Taken from https://image.slidesharecdn.com/vlsisticdaigram-131003215932-phpapp01/95/vlsi-stick-daigram-jce-68-638.jpg?cb=1380837914 (https://image.slidesharecdn.com/vlsisticdaigram-131003215932-phpapp01/95/vlsi-stick-daigram-jce-68-638.jpg?cb=1380837914)

LAYOUTS

The CMOS NAND Gate

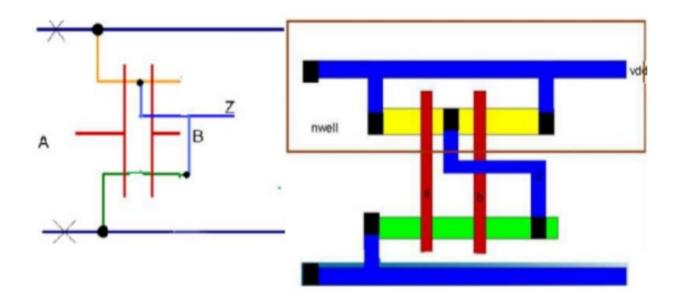

UNIT - II CIRCUIT DESIGN PROCESSES

Taken from https://image.slidesharecdn.com/vlsisticdaigram-131003215932-phpapp01/95/vlsi-stick-daigram-jce-66-638.jpg?cb=1380837914 (https://image.slidesharecdn.com/vlsisticdaigram-131003215932-phpapp01/95/vlsi-stick-daigram-jce-66-638.jpg?cb=1380837914)

The layouts in Virtuoso Layout Suite L can be created as shown in Figure 9a, 9b:

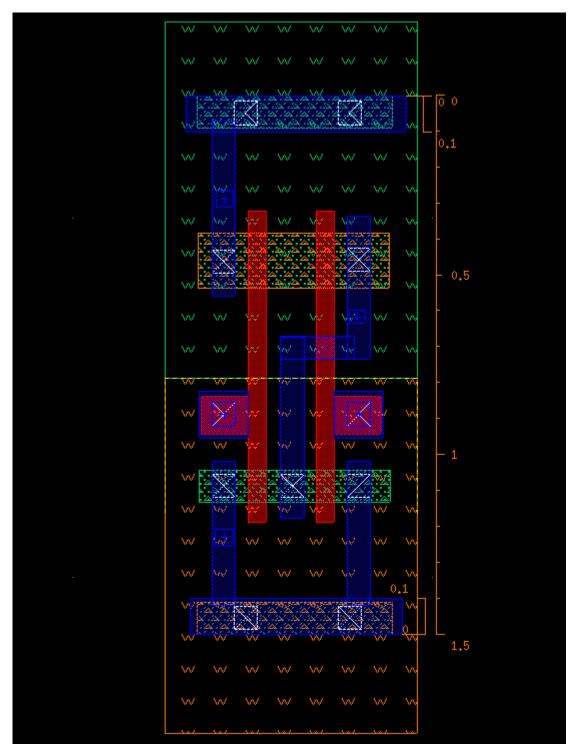


Figure 9a: Layout for NOR gate in Virtuoso Layout Suite L

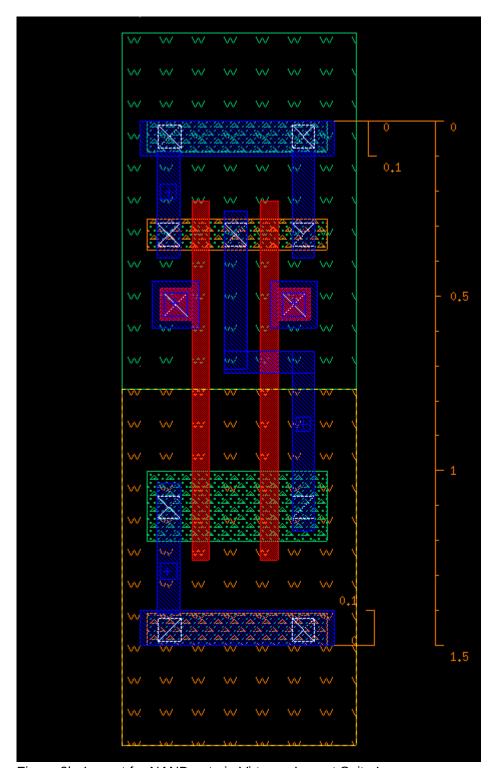


Figure 9b: Layout for NAND gate in Virtuoso Layout Suite L

Physical verification

The physical verification of the 2 layouts are performed using DRC and LVS. The DRC (Figure 10a, 11a) verifies the layout meets all Rules listed in the FreePDK45 process design kit (available at https://www.eda.ncsu.edu/wiki/FreePDK45:Contents (https://www.eda.ncsu.edu/wiki/FreePDK45:Contents)). The LVS (Figure 10b, 11b) verifies that the layout matches the schematics designs shown above.

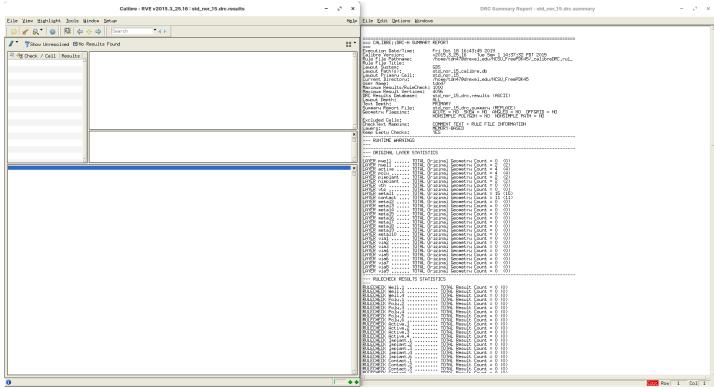


Figure 10a: DRC results for NOR gate layout

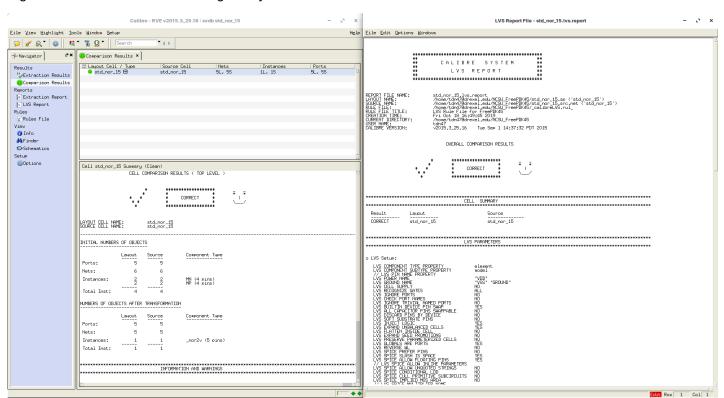


Figure 10b: LVS results for NOR gate layout

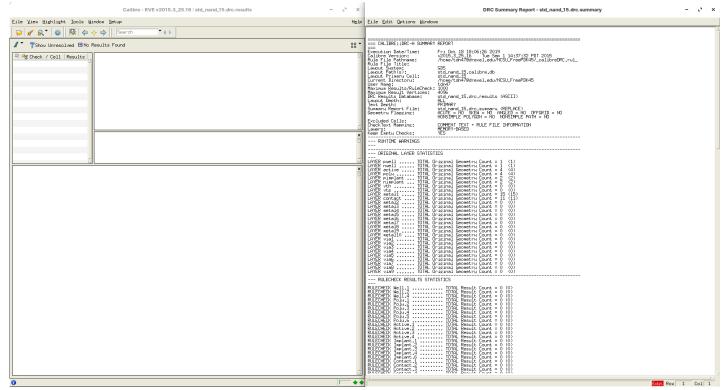


Figure 11a: DRC results for NAND gate layout

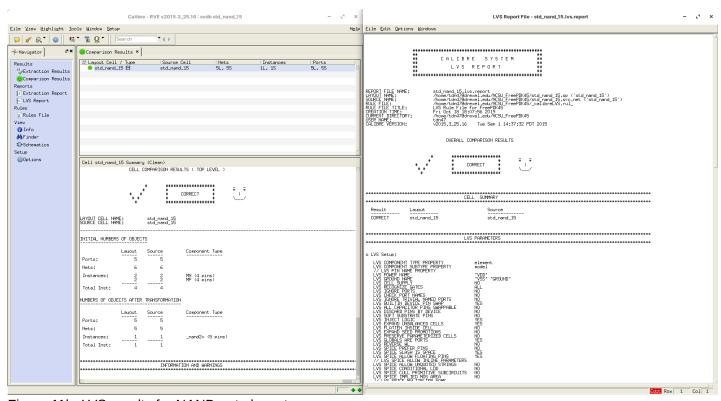


Figure 11b: LVS results for NAND gate layout

Analysis of simulation results:

Propagation delay

In the top level schematic of both gates, the input vpulse have a delay of 0ns, however, in the transient plot, the output does have a delays. The worse ones are recorded above:

$$t_{pdNOR} = 0.07238$$

$$t_{ndNAND} = 0.04752$$

Rise time and Fall time

$$t_{rNOR} = 13.09148 - 13.01852 = 0.07296$$

 $t_{fNOR} = 14.07627 - 14.00903 = 0.06724$
 $t_{rNAND} = 7.05552 - 7.01354 = 0.04198$
 $t_{fNAND} = 8.05000 - 8.00848 = 0.04152$

The rise time and fall time for the NAND gate does not equal <code>exactly</code> because the level of voltage captured at these measurements are different (due to the difficulty in obtaining <code>exact</code> measurement in the software used), but they are very close and could be considered as <code>equal</code>. However, as stated above, the rise time and fall time for the NOR gate are different due to the fact that the software cannot handle an input of 156nm (a restriction of the Rule.Grid.1-6 of the FreePDK45 processing design kit). Hence, a input of 155nm is used, which result in a difference shown above.

Conclusion

The CMOS NOR and NAND gate's circuits and layouts are designed, analyzed and verified in this laboratory. The designing steps involves creating the initial schematics, analyzing worse-case propagation delay through the transient behavior plot, obtaining parametric analysis through the DC plot, select a sizing configuration of the PMOS and NMOS components so as to give symmetric devices, creating the layout and verify such physical layout with DRC and LVS. Finally, the rise time and fall time are observed and recorded as a metric to the performance of both devices.