

# ECEEC-471\571 Introduction to VLSI Design

---

## Lab Assignment #4

### NAND and NOR CMOS Gates

Instructor: Prof. Ioannis Savidis, isavidis@coe.drexel.edu

### Drexel University

### Electrical and Computer Engineering

---

## 1 Objective

The goal of this assignment is to learn how to build a CMOS gate. This assignment will help build an understanding of:

- The basic principles of designing a *Nand* and a *Nor* CMOS gate.
- The characteristics of a *Nand* and a *Nor* CMOS gate.

Note, set the voltage level ( $V_{dd}$ ) for SPICE simulation to 1.2 V. The same voltage level should be used for the input signals to both the NAND and NOR gates.

## 2 Assignments

Design, simulate and build the layout of a **Nand** and a **Nor** CMOS gate.

### 2.1 Design a Nand Gate

1. Design a two input **Nand** gate, where the inputs are labeled **a** and **b**, and the output is labeled **out**. The schematic of the **Nand** gate is shown in Figure 1.
2. Simulate the transient response of the symmetrical **Nand** gate and measure the worst-case propagation delay, rise, and fall times for a pulse input.

Input pulse parameters:

- time period: 2 ns
  - rise time: 5 ps
  - fall time: 5 ps
  - pulse width: 1 ns
3. Simulate the DC response of the **Nand** gate for the worst-case input scenario, and determine the transistor sizing for a symmetrical **Nand** gate
  4. Create the layout view of the **Nand** gate
    - Make sure the total cell height is 1.5  $\mu\text{m}$

- Use  $0.1\ \mu\text{m}$  for the width of the Vdd and Gnd rails
  - A reference for the layout is shown in Figure 2.
5. Perform DRC verification.
  6. Perform LVS verification.

 


Figure 1: A schematic illustration of the *Nand* gate.

## 2.2 Design a Nor Gate

1. Design a two input *Nor* gate, where the inputs are labeled *a* and *b*, and the output is labeled *out*. The schematic of the *Nor* gate is shown in Figure 3.
2. Simulate the transient response of the symmetrical *Nor* gate and measure the worst-case propagation delay, rise, and fall times for a pulse input.  
Input pulse parameters:

 


Figure 2: A layout reference of the *Nand* gate Note: This is a different CMOS technology

- time period: 2 ns
  - rise time: 5 ps
  - fall time: 5 ps
  - pulse width: 1 ns
3. Simulate the DC response of the *Nor* gate for the worst-case input scenario, and determine the transistor sizing for a symmetrical *Nor* gate

4. Create the layout view of the **Nor** gate
  - Make sure the total cell height is  $1.5\ \mu\text{m}$
  - Use  $0.1\ \mu\text{m}$  for the width of the **Vdd** and **Gnd** rails
5. Perform DRC verification.
6. Perform LVS verification.

## 2.3 Deliverables

Your report should include the following:

- The schematic view and the layout view of both the **Nand** gate and the **Nor** gate.
- Show DRC and LVS results for both the **Nand** gate and the **Nor** gate.
- Perform transient simulations on the **Nand** gate and the **Nor** gate to check the functionality, respectively.
- Measure the worst-case propagation delay, rise, and fall time for a pulse input for both the **Nand** and the **Nor** gates based on the simulation results.
- Perform a DC simulation on the schematic view of the **Nand** gate and the **Nor** gate to plot the  $V_{in}$  versus  $V_{out}$  curve. Use markers to show the switching threshold. Find the sizes of the transistors to make the symmetrical version of the **Nand** and the **Nor** gate.

 


Figure 3: A schematic illustration of the *Nor* gate.